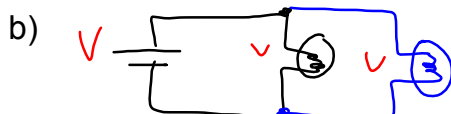


1. What happens to the brightness of the lightbulbs in the following circuits:




2. Draw the following circuit: TWO 9V batteries, with a 10-ohm and 15-ohm connected in series.

a) Calculate total resistance.

b) Calculate current.

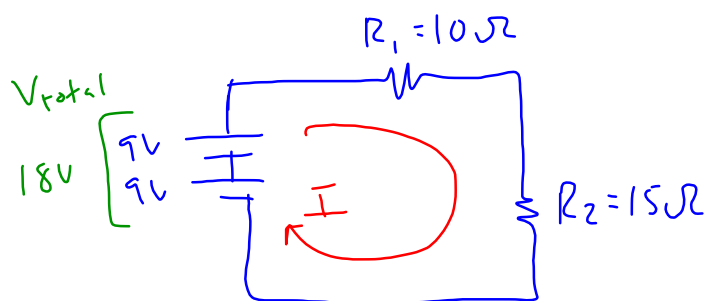c) Calculate voltage across each resistor.



$$\begin{aligned} R_{total} &= R_1 + R_2 \\ &= 10\Omega + 15\Omega \\ &= 25\Omega \end{aligned}$$

$$I = \frac{V_{total}}{R_{total}}$$

$$= \frac{18V}{25V}$$

$$= 0.72A$$


$$V_1 = IR_1 = (0.72A)(10\Omega) = 7.2V$$

$$V_2 = IR_2 = (0.72A)(15\Omega) = 10.8V$$

18V

TWO 9V batteries (in series) are connected in parallel with a 10-ohm and 15-ohm resistor.

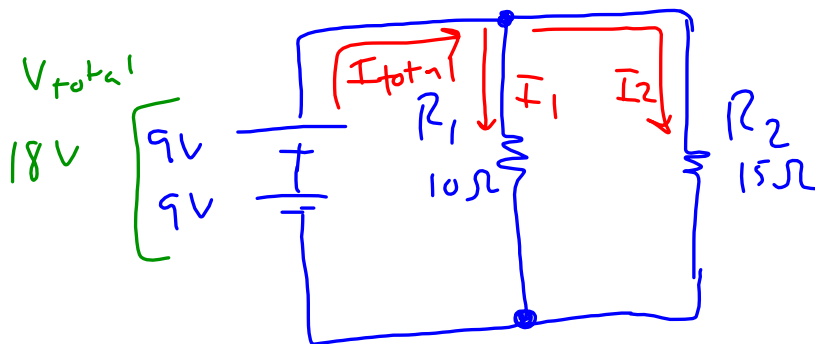- Find the current in each branch.
- Find the total current in the circuit.



$$\begin{aligned}
 I_1 &= \frac{V_{\text{total}}}{R_1} & I_2 &= \frac{V_{\text{total}}}{R_2} \\
 &= \frac{18\text{V}}{10\Omega} & &= \frac{18\text{V}}{15\Omega} \\
 &= 1.8\text{A} & &= 1.2\text{A}
 \end{aligned}$$

$$\begin{aligned}
 I_{\text{total}} &= 1.8\text{A} + 1.2\text{A} \\
 &= 3.0\text{A}
 \end{aligned}$$